

eExam Question Bank

Coursecode:

Choose Coursecode ▼

Show entriesSearch:

<input type="checkbox"/>	Question Type ↕	Question ↕	A ↕	B ↕	C ↕	D ↕	Answer ↕	Remark ↕
<input type="checkbox"/>	FBQ	The NOT gate, OR gate and AND gate are three main types of <input type="text"/>	logic gates	logic gate				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	A <input type="text"/> is a product term that contains all the variables used in a function	minterm					<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	<input type="text"/> is concerned with the interconnection of digital components and modules	Digital Logic					<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	By looking at <input type="text"/> one is able to know the output of any possible combination	truth tables					<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	<input type="text"/> __are set to list the possible inputs and find their corresponding inputs	truth tables					<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	Boolean <input type="text"/> and variable are allowed to have only two possible values	constants					<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	Boolean <input type="text"/> are rules that can help us simplify logic expressions	theorem					<input type="button" value="eExam"/>

<input type="checkbox"/>									
<input type="checkbox"/>	FBQ	A <input type="text"/> is one whose output will change bits state simultaneously, without any ripple.	Synchronous counter						eExam
<input type="checkbox"/>	FBQ	The term <input type="text"/> implies the logical relationship between the inputs and the outputs.	Logic Function						eExam
<input type="checkbox"/>	FBQ	In order to change the state for a bistable element, we need to add external inputs called <input type="text"/> to the circuit	RS latch						eExam
<input type="checkbox"/>	FBQ	SET-CLEAR latch can be called a <input type="text"/>	SET-RESET latch						eExam
<input type="checkbox"/>	FBQ	The D-flip flop is also referred to as the <input type="text"/>	Latch						eExam
<input type="checkbox"/>	FBQ	The operation of an OR gate can be described as a Boolean <input type="text"/>	Addition						eExam
<input type="checkbox"/>	FBQ	The 4-bit input encodes the binary representation of a <input type="text"/> _digit	Decimal						eExam
<input type="checkbox"/>	FBQ	The acronym (IEEE) stands for <input type="text"/>	Institute of Electrical and Electronics Engineers						eExam
<input type="checkbox"/>	FBQ	The universal measuring instrument used extensively in computer laboratory is the <input type="text"/>	Cathode Ray Oscilloscope						eExam
<input type="checkbox"/>	FBQ	The advantage sequential circuits, have over combinational circuits is <input type="text"/>	Timing						eExam

<input type="checkbox"/>									
<input type="checkbox"/>	FBQ	The major differences in these flip-flop types are in the number of _____ they have and how they change states	inputs						eExam
<input type="checkbox"/>	FBQ	The NAND gate is derived from an AND gate and _____ connected in series	Inverter						eExam
<input type="checkbox"/>	FBQ	The Quine-McCluskey or tabulation method for reducing an equation is ideal for _____ the computer	programming						eExam
<input type="checkbox"/>	FBQ	The most universally used logic gate is the _____ gates	NAND						eExam
<input type="checkbox"/>	FBQ	A single latch or flip-flop can store only _____ of information	1-bit	1 bit					eExam
<input type="checkbox"/>	FBQ	The expression for the AND gate output is written _____	A.B						eExam
<input type="checkbox"/>	FBQ	The 4-bit input encodes the binary representation of a _____ digit	decimal						eExam
<input type="checkbox"/>	FBQ	Larger subcubes require fewer _____ because of fewer variables in the product term	AND gates						eExam
<input type="checkbox"/>	FBQ	There are basically four main types of flip-flops: D, S-R, J-K AND _____	T						eExam
<input type="checkbox"/>	FBQ	The Karnaugh map method is an easy way for _____ an equation manually	Reducing						eExam

<input type="checkbox"/>									
<input type="checkbox"/>	FBQ	Hexadecimal numbers require <input type="text"/> different digit symbols	16	sixteen					eExam
<input type="checkbox"/>	FBQ	The NOT gate is also known as the <input type="text"/>	Inverter						eExam
<input type="checkbox"/>	FBQ	A <input type="text"/> is an IC that can be programmed by the user to execute a complex logic function.	PLD						eExam
<input type="checkbox"/>	FBQ	When the hours counter reaches 12, it will be reset to zero by the <input type="text"/> _gate	NAND						eExam
<input type="checkbox"/>	FBQ	One basic piece of test equipment used in digital troubleshooting is the <input type="text"/>	Logic Probe						eExam
<input type="checkbox"/>	FBQ	Whenever both data inputs J and K are at 1, then the flip-flop can be said to be in a <input type="text"/> __state	Toggle						eExam
<input type="checkbox"/>	FBQ	<input type="text"/> _is a prime implicant that includes a 1-minterm that is not included in any other prime implicant	Essential prime implicant						eExam
<input type="checkbox"/>	FBQ	<input type="text"/> gates are widely employed and can be used to make other logic gates	NAND						eExam
<input type="checkbox"/>	FBQ	A Boolean variable is a quantity that may, at different times, be equal to either <input type="text"/>	0 or 1	zero or one					eExam
<input type="checkbox"/>	FBQ	A <input type="text"/> is a term with either a single variable, or two or more variables ORed together	Sum term						eExam

<input type="checkbox"/>									
<input type="checkbox"/>	MCQ	Truth tables for the three basic logical operators are, OR and NOT	ANB	AND	ANM	ANW	B		eExam
<input type="checkbox"/>	MCQ	We write inputs values in the normal binary..... order	serial	system	counting	ascending	C		eExam
<input type="checkbox"/>	MCQ	When dealing with dealing with binary values, each input can be either	a 1 and a 0	a 1 or a 1	0 or a 0	a 0 or a 1	D		eExam
<input type="checkbox"/>	MCQ	The NOT operator is also know as the	octal	truth	inverter	boolean	C		eExam
<input type="checkbox"/>	MCQ	The NOT gate, OR gate and AND gate are three main types of	computer	digital gate	logic gates	All gates	C		eExam
<input type="checkbox"/>	MCQ	The ----- principle states that if a boolean expression is 'True', then, its dual is 'True'	system	duality	duolity	truth	B		eExam
<input type="checkbox"/>	MCQ	When counting in octal, the number after 7 is	0 to 7	8	9	10	D		eExam
<input type="checkbox"/>	MCQ	Since octal is base-8 and hexadecimal is base	14	16	18	12	B		eExam
<input type="checkbox"/>	MCQ	The use of ----- is quite familiar to us	binary	digit	decimal	a bit	C		eExam
<input type="checkbox"/>	MCQ	To build ----- devices that can process these values accurately is next to impossible	world	analog	digital	system	B		eExam
<input type="checkbox"/>	MCQ	----- circuits deal with binary values	binary	truth table	Boolean	inputs	A		eExam
<input type="checkbox"/>	MCQ	A combinational circuit can be described precisely by	operations	truth table	function	symbols	B		eExam
<input type="checkbox"/>	MCQ	----- circuits whose outputs are dependent on not only the current input	gate	combinational	boolean	sequential	D		eExam
<input type="checkbox"/>	MCQ	----- circuit are dependent only on the current inputs	electric	combinational	system	gate	B		eExam
<input type="checkbox"/>	MCQ	We use special logic ----- ---- to denote the gates	signs	arrows	symbols	directions	C		eExam
<input type="checkbox"/>	MCQ	In drawing digital circuit diagrams are also called ---	symbols	inverter	schematics	gate	C		eExam

<input type="checkbox"/>								
<input type="checkbox"/>	MCQ	The name ----- comes from the fact that these devices operate like a door	or gate	gate	window	system	B	eExam
<input type="checkbox"/>	MCQ	----- is a circuit that operates such that its output is high only when all input are high	or gate	AND gate	NOT gate	all gate	B	eExam
<input type="checkbox"/>	MCQ	There are basically the AND gate, OR gate and NOT gate also known as --- -----	logic gates	inverter	all gates	system gates	B	eExam
<input type="checkbox"/>	MCQ	----- are the actual physical implementations of logical operators	truth table	logic gates	gates	binary gates	B	eExam
<input type="checkbox"/>	MCQ theorems are extremely useful in simplifying expression	Boolean	barth	DeMorgan	Nneji	C	eExam
<input type="checkbox"/>	MCQ	Two of the most important theorems of boolean algebra were contributed by	Morgan	Onashoga	JP Morgan	DeMorgan	D	eExam
<input type="checkbox"/>	MCQ	Boolean algebra is a tool for the analysis and design of ----- system	binary	digit	digital	computer	C	eExam
<input type="checkbox"/>	MCQ	The NAND gate is formed from the combination of the AND gate and _____ connected in series	OR	NOR	XOR	NOT	D	eExam
<input type="checkbox"/>	MCQ	The most important memory element is the flip-flop, which is made up of an assembly of _____	NOR gate	OR gate	logic gates	AND gate	C	eExam
<input type="checkbox"/>	MCQ	The output of the MOD-6 counter in the MINUTES section has a frequency of _____	1 pulse per min	1 pulse per hour	1 pulse per sec	2 pulse per sec	B	eExam
<input type="checkbox"/>	MCQ	If we connect two switches in parallel, this gives rise to the logical _____ operator	NOR	NOT	AND	OR	D	eExam
<input type="checkbox"/>	MCQ	When the hours counter reaches 12, it will be reset to zero by the _____ gate	AND	NAND	NOR	OR	B	eExam
<input type="checkbox"/>	MCQ	A Bistable element is the simplest _____ circuit	Processing	Control	Storage	Inverting	C	eExam

<input type="checkbox"/>								
<input type="checkbox"/>	MCQ	The binary number 1000001010 equals _____ in decimal	522	520	500	501	A	eExam
<input type="checkbox"/>	MCQ	The K-map is a _____ array of squares.	1-dimensional	2-dimensional	3-dimensional	4-dimensional	B	eExam
<input type="checkbox"/>	MCQ	The K-map method reduces a Boolean function from its canonical form to its _____ form	subcubes	Trackball	cube	standard	D	eExam
<input type="checkbox"/>	MCQ	The BCD Up-down Counter counts from _____	0 to 2	0 to 7	0 to 9	0 to 3	C	eExam
<input type="checkbox"/>	MCQ	The exclusive-OR gate is another logic gate which can be constructed using _____	AND	OR	NOT	all of the above	D	eExam
<input type="checkbox"/>	MCQ	The BCD does not use the numbers 1010, 1011, 1100, 1101, 1110 and 1111	True	False	not sure	none of the options	A	eExam
<input type="checkbox"/>	MCQ	Covert 101 111 010 100 base 2 to base 8	5724	5725	5624	5734	A	eExam
<input type="checkbox"/>	MCQ	Complex Boolean equations can be simplified by a new kind of algebra, which is popularly called _____	linear algebra	complex algebra	switching algebra	none above	C	eExam
<input type="checkbox"/>	MCQ	Which of these electronic components are connected together to form logic gates.	Capacitors	Transistors	Resistors	Thyristor	B	eExam
<input type="checkbox"/>	MCQ	if $x=0$, $y=1$, $z=0$. the Logic gate 3-OR ($X+Y+Z$) in the truth table will be ?	10	not sure	0	1	D	eExam
<input type="checkbox"/>	MCQ	Transistors, acting as tiny electronic binary switches are connected together to form logic gates	True	False	not sure	all of the above	A	eExam
<input type="checkbox"/>	MCQ	The decimal value for the binary number 1011011 is	91	191	82	67	A	eExam
<input type="checkbox"/>	MCQ	In Logic, the circuit that operates such that its output is high only when all its inputs are high is called?	the OR gate	the NAND gate	the NOR gate	the AND gate	D	eExam
<input type="checkbox"/>	MCQ	What will be the output of a 2-input (x & y) NAND gate, if $x = 0$, $y = 1$	High	Toggle	Low	Forbidden	A	eExam

<input type="checkbox"/>								
<input type="checkbox"/>	MCQ	what will be the output of a 3-input AND gate(X,Y,Z), if X = 0, Y= 1, Z = 1?	10	0	1	101	B	eExam
<input type="checkbox"/>	MCQ	The decimal value for the binary number 1011011 is	91	97	192	45	A	eExam
<input type="checkbox"/>	MCQ	Which of these theorem is useful in converting maxterm-to-miniterm and miniterm-to-maxterm Boolean expression	Karnaugh Map Theorem	De Morgan's Theorem	Boolean Theorem	None of the option	B	eExam
<input type="checkbox"/>	MCQ	Covert 101 111 010 100 base 2 to base 8	5723	5744	524	5724	D	eExam
<input type="checkbox"/>	MCQ	Which of these is a circuit simulator used to accurately convert Boolean expression to Truth table or otherwise	Digital Converter	Electronic Workbench	Mathlab	Logical Converter	B	eExam
<input type="checkbox"/>	MCQ	Covert the octal number 5724 to base 2	101 111 010 101	101 111 010 100	101 101 010 100	101 111 010 110	B	eExam
<input type="checkbox"/>	MCQ	Which logic gate complements the input?	AND	OR	NAND	NOT	D	eExam
<input type="checkbox"/>	MCQ	Whenever the J-K flip-flop is wired for use only in the toggle mode, then the flip-flop is commonly called	Clocked JK flip-flop	T flip-flop	Toggled JK flip-flop	D flip-flop	B	eExam
<input type="checkbox"/>	MCQ	Which logic gate might be called the " any but not all gate?"	NAND	XOR	OR	XNOR	B	eExam
<input type="checkbox"/>	MCQ	Which logic gate might be called the " any or all gate"?	NAND	XOR	OR	XNOR	C	eExam
<input type="checkbox"/>	MCQ	Which logic gate might be called the " all or nothing gate"?	NAND	XOR	OR	XNOR	D	eExam
<input type="checkbox"/>	MCQ	Switches arranged in series will act like what type of logic gate?	OR	AND	NOT	NAND	B	eExam
<input type="checkbox"/>	MCQ	Switches arranged in parallel will act like what type of logic gate?	OR	AND	NOT	NAND	A	eExam
<input type="checkbox"/>	MCQ	Tiny electronic binary switches that are connected together to form logic gates are called?	Transformer	capacitors	Resistors	Transistors	D	eExam
<input type="checkbox"/>	MCQ	A minterm is a product term that contains all the variables used in a function	False	not sure	True	none above	C	eExam

<input type="checkbox"/>								
<input type="checkbox"/>	MCQ	The Binary Coded Decimal does not support four bit	True	False	All of the above	None of the above	A	eExam
<input type="checkbox"/>	MCQ	Covert this octal number 5724 to binary numbering system	111 101 001 110	101 111 010 101	101 101 010 100	101 111 010 100	D	eExam
<input type="checkbox"/>	MCQ	What range of number is the Octal numbering system?	0 to 8	1 to 8	0 to 7	0 to 10	C	eExam

Showing 1 to 120 of 120 entries

[Previous](#) [1](#) [Next](#)