

eExam Question Bank

Coursecode:

Show entriesSearch:

<input type="checkbox"/>	Question Type ↓↑	Question ↑↓	A ↑↓	B ↑↓	C ↑↓	D ↑↓	Answer ↑↓	Remark ↑↓
<input type="checkbox"/>	FBQ	A type of rechargeable cell in common use for electrical experiments in the laboratory, which can supply relatively constant voltage and current for a relatively longer period of time is called <input type="text"/>	accumulator	accumulator				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	A student designed a circuit which consisted of two variable resistors P and Q, two cells E1 and E2 of negligible internal resistance and a galvanometer. He connected E1 across the series combination of P and Q and then connects the series combination of the cell E2 and the galvanometer across P. He adjusted the variable resistances to obtain a null condition of the galvanometer. The ratio of the emf of E2 to that of E1 is <input type="text"/> (You may choose your answer from the list: P/Q, (P+Q)/Q, P/(P+Q), Q/(P+Q))	$P/(P+Q)$	$P/(P+Q)$				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	In the absence of a slider contact a <input type="text"/> clip may be used in experiments involving the use of metre bridge	crocodile	crocodile				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	In an experiment to determine the internal resistance r of a dry cell using the potentiometer, the resistance box was used to provide different values of the external resistance R in the circuit. A graph of $1/R$ against <input type="text"/> was plotted to obtain a straight line of the form $y = mx + c$, where $m = l_1/l_2$, l_1 and l_2 being the balance lengths for open and closed circuits respectively. The intercept on the horizontal axis when $1/R = 0$ is used to find the internal resistance for the cell	$1/r$	$1/r$				<input type="button" value="eExam"/>

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	In an experiment involving two resistances in series, the slope of the graph of V against I represents <input type="text"/>	equivalent resistance	equivalent resistance				eExam
<input type="checkbox"/>	FBQ	For a metallic conductor, Ohm's law holds provided <input type="text"/> , pressure and other physical factors remains constant	temperature	temperature				eExam
<input type="checkbox"/>	FBQ	When plotting straight line graphs of experimental data, the line is referred to as line of <input type="text"/>	bestfit	bestfit				eExam
<input type="checkbox"/>	FBQ	An electrical source with internal resistance r is used to operate a lamp of resistance R . The fraction of the total power delivered to the lamp is <input type="text"/> . You may choose your answer from: $(r+R)/R$, $(r+R)/r$, $R/(r+R)$, R/r	$R/(r+R)$	$R/(r+R)$				eExam
<input type="checkbox"/>	FBQ	Another means of introducing variable resistance into a circuit instead of resistance wire is to use <input type="text"/> box	resistance	resistance				eExam
<input type="checkbox"/>	FBQ	A 3V- battery with internal resistance of 0.5Ω is connected across a parallel combination of a $1\text{-}\Omega$ and $2\text{-}\Omega$ resistances. The current in the $2\text{-}\Omega$ resistance is <input type="text"/> A to 2 decimal places	0.91	0.91				eExam
<input type="checkbox"/>	FBQ	In an experiment, $\frac{V}{I}$ is plotted against $\frac{1}{I}$. The physical significance of the slope of the graph is <input type="text"/>	conductance	conductance				eExam
<input type="checkbox"/>	FBQ	A $1\text{ m}\Omega$ resistor is to be made from a 1-mm diameter wire of resistivity $2.8 \times 10^{-8} \Omega\text{m}$. The length of the wire to one place of decimal is <input type="text"/> cm	2.8	2.8				eExam
<input type="checkbox"/>	FBQ	Two resistances of 2Ω each are connected in parallel and then connected in series to a 1Ω resistance. The equivalent resistance is <input type="text"/> Ω	2	two				eExam
<input type="checkbox"/>	FBQ	Kirchoff's loop rule represents conservation of <input type="text"/>	energy	energy				eExam

<input type="checkbox"/>									
<input type="checkbox"/>	FBQ	The relation between the current I , through the heated filament and the applied voltage, V , is given by the general form $I = KV^n$, where K and n are constants. For the empirical relationship between I and V , a straight line graph is plotted from the relation $\log I =$ <input type="text"/>	$n \log V + \log K$	$\log K + n \log V$					eExam
<input type="checkbox"/>	FBQ	The slide wire of the figure shown is balanced when the the uniform slide wire AB is divided as shown. The value of the resistance X is <input type="text"/> Ω	2	two					eExam
<input type="checkbox"/>	FBQ	The diagram shown is called a <input type="text"/>	metre bridge	Wheatstone bridge					eExam
<input type="checkbox"/>	FBQ	The device shown is called <input type="text"/>	Wheatstone bridge	Wheatstone bridge					eExam
<input type="checkbox"/>	FBQ	The difference between the emf of a battery and the lost volts when discharging is called <input type="text"/> potential difference or voltage	terminal	terminal					eExam
<input type="checkbox"/>	FBQ	Resistances in series have the same <input type="text"/>	current	current					eExam
<input type="checkbox"/>	FBQ	In the circuit shown, the name of the device which provides silding contact with the resistance wire PQ is called <input type="text"/>	jockey	jockey					eExam
<input type="checkbox"/>	FBQ	A <input type="text"/> cell such Weston cadmium cell is used in a suitable circuit to determine the emf of unknown cell	standard	standard					eExam
<input type="checkbox"/>	FBQ	To change a galvanometer to a voltmeter, connect a high resistance in <input type="text"/> to it	series	series					eExam
<input type="checkbox"/>	FBQ	In the circuit shown, the wire PQ is usually made up of a material called <input type="text"/>	constantan	constantan					eExam
<input type="checkbox"/>	FBQ	In the circuit diagram shown, the device marked X is a <input type="text"/>	galvanometer	galvanometer					eExam

<input type="checkbox"/>									
<input type="checkbox"/>	FBQ	In the circuit diagram shown, the wire PQ has the resistance of 5Ω and the driver cell has an emf of 2.00 V. The value of the resistance R if a balance point is obtained at 0.600 m along PQ when measuring an emf of 6.00mV? is <input type="text"/> (Leave your answer to the nearest whole number)	995	995					eExam
<input type="checkbox"/>	FBQ	The null condition in experiments involving the use of the device shown implies that the <input type="text"/> s are balanced	potential difference	voltage					eExam
<input type="checkbox"/>	FBQ	The advantage of the device shown over the voltmeter in measurements of emf is that it does NOT draw <input type="text"/> from the cell or battery under test	electric current	current					eExam
<input type="checkbox"/>	FBQ	The figure shown is the circuit diagram of a <input type="text"/>	potentiometer	potentiometer					eExam
<input type="checkbox"/>	FBQ	In the construction of an ammeter, a low resistance called <input type="text"/> resistance is connected in parallel to a suitable galvanometer	shunt	shunt					eExam
<input type="checkbox"/>	FBQ	The same electric <input type="text"/> flows through resistors connected in series	current	current					eExam
<input type="checkbox"/>	FBQ	A device known as <input type="text"/> may be used for comparison of resistances	Wheatstone bridge	metre bridge					eExam
<input type="checkbox"/>	FBQ	A device which may be used to compare the potential differences of electric cells is <input type="text"/>	potentiometer	potentiometer					eExam
<input type="checkbox"/>	FBQ	The equivalent resistance of a 2Ω and a 3Ω resistances in parallel is <input type="text"/> Ω	6/5	1.2					eExam
<input type="checkbox"/>	FBQ	The term "lost volts" is used to describe the energy dissipated in the <input type="text"/> of a source of electromotive force	internal resistance	internal resistance					eExam
<input type="checkbox"/>	FBQ	Resistances in parallel have the same <input type="text"/>	potential difference	voltage					eExam

<input type="checkbox"/>									
<input type="checkbox"/>	FBQ	<input type="text"/> is defined as the time rate of flow of charge across a unit cross-sectional area of a conductor	electric current	Electric current					eExam
<input type="checkbox"/>	FBQ	The ratio $V/I =$ <input type="text"/> (The symbols have their usual meaning)	R	R					eExam
<input type="checkbox"/>	FBQ	Beyond the critical angle a ray of light moving from dense to rare medium suffers <input type="text"/>	total internal reflection	total internal reflection					eExam
<input type="checkbox"/>	FBQ	The bending of a ray of light as it travels from one transparent medium to another is called <input type="text"/>	refraction	refraction					eExam
<input type="checkbox"/>	FBQ	For the refraction through the triangular glass prism, $d-e$ was plotted on the vertical axis against i on the horizontal axis according to the equation $d-e = i-A$ and the symbols have their usual meaning. The graph obtained is a straight line and the intercept on the i -axis is <input type="text"/>	A	A					eExam
<input type="checkbox"/>	FBQ	A lens which is thinner at centre than at the edge is a <input type="text"/> lens	diverging	concave					eExam
<input type="checkbox"/>	FBQ	When an object is placed in front of a convex lens L between F' and $2F'$, a <input type="text"/> and inverted image is formed	real	real					eExam
<input type="checkbox"/>	FBQ	For concave mirrors, the object distance is always <input type="text"/> (Choose from: positive, negative)	positive	positive					eExam
<input type="checkbox"/>	FBQ	The image of an object placed between the focal point and the pole of a concave mirror is behind the mirror, erect, enlarged and <input type="text"/>	virtual	virtual					eExam
<input type="checkbox"/>	FBQ	Given the radius of curvature R of a spherical mirror, the mirror equation can be written in terms of the object distance u and image distance v as $\frac{1}{u} + \frac{1}{v} = \frac{x}{R}$. X is <input type="text"/>	2	2					eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	In an experiment, based on the equation $\mu = \frac{\sin i}{\sin r}$, $\sin i$ was plotted on the vertical axis and $\sin r$ on the horizontal axis. Then, μ is the <input type="text"/> of the graph.	slope	gradient				eExam
<input type="checkbox"/>	FBQ	The equation $\mu = \frac{\sin i}{\sin r}$, where the symbols have their usual meaning is called <input type="text"/> 's law	Snell	Snell				eExam
<input type="checkbox"/>	FBQ	In the equation $\mu = \frac{\sin i}{\sin r}$, where i and r are the angles of incidence and refraction respectively, μ is called the <input type="text"/>	refractive index	index of refraction				eExam
<input type="checkbox"/>	FBQ	The bending of a ray of light as it passes from one medium to another is called <input type="text"/>	refraction	refraction				eExam
<input type="checkbox"/>	FBQ	A type of rechargeable cell in common use for electrical experiments in the laboratory, which can supply relatively constant voltage and current for a relatively longer period of time is called <input type="text"/>	accumulator	accumulator				
<input type="checkbox"/>	FBQ	A student designed a circuit which consisted of two variable resistors P and Q , two cells E_1 and E_2 of negligible internal resistance and a galvanometer. He connected E_1 across the series combination of P and Q and then connects the series combination of the cell E_2 and the galvanometer across P . He adjusted the variable resistances to obtain a null condition of the galvanometer. The ratio of the emf of E_2 to that of E_1 is <input type="text"/> (You may choose your answer from the list: P/Q , $(P+Q)/Q$, $P/(P+Q)$, $Q/(P+Q)$)	$P/(P+Q)$	$P/(P+Q)$				
<input type="checkbox"/>	FBQ	In the absence of a slider contact a <input type="text"/> clip may be used in experiments involving the use of metre bridge	crocodile	crocodile				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	In an experiment to determine the internal resistance r of a dry cell using the potentiometer, the resistance box was used to provide different values of the external resistance R in the circuit. A graph of $1/R$ against <input type="text"/> was plotted to obtain a straight line of the form $y = mx + c$, where $m = l_1/l_2$, l_1 and l_2 being the balance lengths for open and closed circuits respectively. The intercept on the horizontal axis when $1/R = 0$ is used to find the internal resistance for the cell	$1/r$	$1/r$				
<input type="checkbox"/>	FBQ	In an experiment involving two resistances in series, the slope of the graph of V against I represents <input type="text"/>	equivalent resistance	equivalent resistance				
<input type="checkbox"/>	FBQ	For a metallic conductor, Ohm's law holds provided <input type="text"/> , pressure and other physical factors remains constant	temperature	temperature				
<input type="checkbox"/>	FBQ	When plotting straight line graphs of experimental data, the line is referred to as line of <input type="text"/>	bestfit	bestfit				
<input type="checkbox"/>	FBQ	An electrical source with internal resistance r is used to operate a lamp of resistance R . The fraction of the total power delivered to the lamp is <input type="text"/> . You may choose your answer from: $(r+R)/R$, $(r+R)/r$, $R/(r+R)$, R/r	$R/(r+R)$	$R/(r+R)$				
<input type="checkbox"/>	FBQ	Another means of introducing variable resistance into a circuit instead of resistance wire is to use <input type="text"/> box	resistance	resistance				
<input type="checkbox"/>	FBQ	A 3V- battery with internal resistance of $0.5\ \Omega$ is connected across a parallel combination of a $1\ \Omega$ and $2\ \Omega$ resistances. The current in the $2\ \Omega$ resistance is <input type="text"/> A to 2 decimal places	0.91	0.91				
<input type="checkbox"/>	FBQ	In an experiment, $\frac{1}{V}$ is plotted against $\frac{1}{I}$. The physical significance of the slope of the graph is <input type="text"/>	conductance	conductance				

<input type="checkbox"/>							
<input type="checkbox"/>	FBQ	A 1 m Ω resistor is to be made from a 1-mm diameter wire of resistivity $2.8 \times 10^{-8} \Omega\text{m}$. The length of the wire to one place of decimal is <input type="text"/> cm	2.8	2.8			
<input type="checkbox"/>	FBQ	Two resistances of 2 Ω each are connected in parallel and then connected in series to a 1 Ω resistance. The equivalent resistance is <input type="text"/> Ω	2	two			
<input type="checkbox"/>	FBQ	Kirchoff's loop rule represents conservation of <input type="text"/>	energy	energy			
<input type="checkbox"/>	FBQ	The relation between the current I, through the heated filament and the applied voltage, V, is given by the general form $I = KV^n$, where K and n are constants. For the empirical relationship between I and V, a straight line graph is plotted from the relation $\log I =$ <input type="text"/>	$n \log V + \log K$	$\log K + n \log V$			
<input type="checkbox"/>	FBQ	The slide wire of the figure shown is balanced when the the uniform slide wire AB is divided as shown. The value of the resistance X is <input type="text"/> Ω	2	two			
<input type="checkbox"/>	FBQ	The diagram shown is called a <input type="text"/>	metre bridge	Wheatstone bridge			
<input type="checkbox"/>	FBQ	The device shown is called <input type="text"/>	Wheatstone bridge	Wheatstone bridge			
<input type="checkbox"/>	FBQ	The difference between the emf of a battery and the lost volts when discharging is called <input type="text"/> potential difference or voltage	terminal	terminal			
<input type="checkbox"/>	FBQ	Resistances in series have the same <input type="text"/>	current	current			
<input type="checkbox"/>	FBQ	In the circuit shown, the name of the device which provides sliding contact with the resistance wire PQ is called <input type="text"/>	jockey	jockey			
<input type="checkbox"/>	FBQ	A <input type="text"/> cell such Weston cadmium cell is used in a suitable circuit to determine the emf of unknown cell	standard	standard			

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	To change a galvanometer to a voltmeter, connect a high resistance in <input type="text"/> to it	series	series				
<input type="checkbox"/>	FBQ	In the circuit shown, the wire PQ is usually made up of a material called <input type="text"/>	constantan	constantan				
<input type="checkbox"/>	FBQ	In the circuit diagram shown, the device marked X is a <input type="text"/>	galvanometer	galvanometer				
<input type="checkbox"/>	FBQ	In the circuit diagram shown, the wire PQ has the resistance of 5Ω and the driver cell has an emf of 2.00 V. The value of the resistance R if a balance point is obtained at 0.600 m along PQ when measuring an emf of 6.00mV? is <input type="text"/> (Leave your answer to the nearest whole number)	995	995				
<input type="checkbox"/>	FBQ	The null condition in experiments involving the use of the device shown implies that the <input type="text"/> s are balanced	potential difference	voltage				
<input type="checkbox"/>	FBQ	The advantage of the device shown over the voltmeter in measurements of emf is that it does NOT draw <input type="text"/> from the cell or battery under test	electric current	current				
<input type="checkbox"/>	FBQ	The figure shown is the circuit diagram of a <input type="text"/>	potentiometer	potentiometer				
<input type="checkbox"/>	FBQ	In the construction of an ammeter, a low resistance called <input type="text"/> resistance is connected in parallel to a suitable galvanometer	shunt	shunt				
<input type="checkbox"/>	FBQ	The same electric <input type="text"/> flows through resistors connected in series	current	current				
<input type="checkbox"/>	FBQ	A device known as <input type="text"/> may be used for comparison of resistances	Wheatstone bridge	metre bridge				
<input type="checkbox"/>	FBQ	A device which may be used to compare the potential differences of electric cells is <input type="text"/>	potentiometer	potentiometer				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	The equivalent resistance of a $2\ \Omega$ and a $3\ \Omega$ resistances in parallel is <input type="text"/> Ω	6/5	1.2				
<input type="checkbox"/>	FBQ	The term "lost volts" is used to describe the energy dissipated in the <input type="text"/> of a source of electromotive force	internal resistance	internal resistance				
<input type="checkbox"/>	FBQ	Resistances in parallel have the same <input type="text"/>	potential difference	voltage				
<input type="checkbox"/>	FBQ	<input type="text"/> is defined as the time rate of flow of charge across a unit cross-sectional area of a conductor	electric current	Electric current				
<input type="checkbox"/>	FBQ	The ratio $V/I =$ <input type="text"/> (The symbols have their usual meaning)	R	R				
<input type="checkbox"/>	FBQ	Beyond the critical angle a ray of light moving from dense to rare medium suffers <input type="text"/>	total internal reflection	total internal reflection				
<input type="checkbox"/>	FBQ	The bending of a ray of light as it travels from one transparent medium to another is called <input type="text"/>	refraction	refraction				
<input type="checkbox"/>	FBQ	For the refraction through the triangular glass prism, $d-e$ was plotted on the vertical axis against i on the horizontal axis according to the equation $d-e = i-A$ and the symbols have their usual meaning. The graph obtained is a straight line and the intercept on the i -axis is <input type="text"/>	A	A				
<input type="checkbox"/>	FBQ	A lens which is thinner at centre than at the edge is a <input type="text"/> lens	diverging	concave				
<input type="checkbox"/>	FBQ	When an object is placed in front of a convex lens L between F' and $2F'$, a <input type="text"/> and inverted image is formed	real	real				
<input type="checkbox"/>	FBQ	For concave mirrors, the object distance is always <input type="text"/> (Choose from: positive, negative)	positive	positive				
<input type="checkbox"/>	FBQ	The image of an object placed between the focal point and the pole of a concave mirror is behind the mirror, erect, enlarged and <input type="text"/>	virtual	virtual				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	Given the radius of curvature R of a spherical mirror, the mirror equation can be written in terms of the object distance u and image distance v as $\frac{1}{u} + \frac{1}{v} = \frac{1}{R}$. X is <input type="text"/>	2	2				
<input type="checkbox"/>	FBQ	In an experiment, based on the equation $\mu = \frac{\sin i}{\sin r}$, μ was plotted on the vertical axis and $\sin r$ on the horizontal axis. Then, μ is the <input type="text"/> of the graph.	slope	gradient				
<input type="checkbox"/>	FBQ	The equation $\mu = \frac{\sin i}{\sin r}$, where the symbols have their usual meaning is called <input type="text"/> 's law	Snell	Snell				
<input type="checkbox"/>	FBQ	In the equation $\mu = \frac{\sin i}{\sin r}$, where i and r are the angles of incidence and refraction respectively, μ is called the <input type="text"/>	refractive index	index of refraction				
<input type="checkbox"/>	FBQ	The bending of a ray of light as it passes from one medium to another is called <input type="text"/>	refraction	refraction				
<input type="checkbox"/>	MCQ	The advantage of potentiometer over voltmeter in measurements of emf is that	the potentiometer wire is assumed to be uniform	it does not draw current from the circuit under test	the temperature of the wire must remain constant	faults may arise due to breaks or wrong connections in the circuit	B	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	Which of these is not a useful precaution in an electrical experiment?	key should be removed between readings to avoid battery run-down	jockeys should be dragged on resistance wires	the connections in the circuit should be tight	readings should be recorded as soon as they are obtained	B	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	Which of the following is NOT true about a rheostat?	It is a constant current instrument	It is a resistor with moving contact	It is used for varying the current in a circuit	It is used for varying the resistance in a circuit	A	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	In an experiment, potential difference is plotted on the vertical axis and current on the horizontal axis. The slope of the graph represents	resistivity	conductivity	resistance	conductance	C	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	For a metallic conductor, Ohm's law holds provided	potential difference varies	current remains constant	temperature remains constant	potential difference remains constant	C	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The lens of the human eye is	concave	converging	planconcave	diverging	B	<input type="button" value="eExam"/>

<input type="checkbox"/>	MCQ	Which of the following precautions is NOT applicable to experiment involving planoconvex lens?	planoconvex lens should have small focal length	parallax error should be avoided	the surface of the lens should be cleaned properly	the tip of the optical pin should be at the same level with the principal axis of the lens	A	eExam
<input type="checkbox"/>	MCQ	A glass prism of refracting angle 60 degrees gives a minimum deviation of 47degrees. What is the refractive index of the glass?	1.61	1.20	1.52	1.41	A	eExam
<input type="checkbox"/>	MCQ	Calculate the distance and magnification of an object placed 20cm from a converging lens	60cm and 0.3 times the size of object	20cm and 0.3 times the size of object	60cm and 3 times the size of object	80cm and 3 times the size of object	D	eExam
<input type="checkbox"/>	MCQ	diopeter measures	linear magnification of lens	power of lens	inverse of object distance from lens	inverse of image distnce from lens	C	eExam
<input type="checkbox"/>	MCQ	Which of the following is not true about diverging lens	the principal focus is positive	the principal focus is ngative	they poudce virtual images only	they form virtual, erect and smaller images of real object	B	eExam
<input type="checkbox"/>	MCQ	In an experiment to determine the focal length of a convex lens, $1/u$ (cm^{-1}) was plotted on horizontal and $1/v$ (cm^{-1}) on the vertical axis, where u and v have their usual meaning. What is the physical significance of the reciprocal of the intercept on the horizontal axis?	linear magnification	focal length	object distance	image distance	C	eExam
<input type="checkbox"/>	MCQ	In an experiment to determine the focal length of a convex lens, $1/u$ (cm^{-1}) was plotted on horizontal and $1/v$ (cm^{-1}) on the vertical axis, where u and v have their usual meaning. What is the physical significance of the reciprocal of the slope of the graph?	linear magnification	focal length	object distance	image distance	A	eExam
<input type="checkbox"/>	MCQ	In practical experiment inolving the use of optical pins, parallax is reduced or removed if on slightly displacing one's eye from side to side	the object and image are not coincident but move together in same directions	the object and image move in opposite directions relative to each other	the object and image are coincident and move together in the same direction	the object and image are coincident and remain stationary	C	eExam
<input type="checkbox"/>	MCQ	In an experiment with a concave mirror, the image of an optical pin which is 4 times its size was cast on on a screen 6m from the object pin. How far from the object pin should the mirror be placed?	8m	6m	3m	2m	D	eExam

<input type="checkbox"/>	MCQ	The image of an object which is between the concave mirror's reflecting surface and its principal focus is	in front of the mirror erect real and diminished	behind the mirror inverted real and diminished	in front of the mirror erect virtual and enlarged	behind the mirror erect virtual and enlarged	D	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The bending of a ray of light as it travels from one transparent medium to another is called -----	reflection	polarisation	refraction	diffraction	C	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	In the construction of an ammeter, a low resistance called resistance----- is connected in parallel to a suitable galvanometer	multiplier	shunt	milliammeter	galvanometer	B	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The unit of electrical energy expended per unit time is called -----	joule	ampere	volt	watt	D	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The name of the device which provides sliding contact with the potentiometer wire is called -----	jockey	rheostat	galvanometer	meter bridge	A	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The difference between the emf of a battery and the lost volts when discharging is called	electromotive force	terminal voltage	internal resistance	lost power	B	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	A device known as ----- may be used for comparison of resistances	Wheatstone bridge	potentiometer	voltmeter	rheostat	A	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	A device which may be used to compare the potential differences of electric cells is called -----	metre bridge	wheatstone bridge	rheostat	potentiometer	D	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The term "lost volts" is used to describe ----- of a cell	electromotive force	terminal potential difference	energy dissipated in the internal resistance	total current	C	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	The time rate of flow of charge across a unit cross-sectional area of a conductor defines	potential difference	electromotive force	electrical resistance	electric current	D	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	A $1\text{ m}\Omega$ resistor is to be made from a 1-mm diameter wire of resistivity 2.8×10^{-8} . Find the length of the wire	4.2cm	3.6cm	2.8cm	1.4cm	C	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	Which of the following is correct?	Kirchoff's junction rule represents conservation of momentum	Kirchoff's loop rule represents conservation of charge	Kirchoff's loop rule represents conservation of energy	Kirchoff's junction rule represents conservation of energy	C	<input type="button" value="eExam"/>
<input type="checkbox"/>	MCQ	Two resistances of 2Ω each are connected in parallel and then connected in series to a 1Ω resistance. What is the equivalent resistance	1Ω	2Ω	3Ω	4Ω	B	<input type="button" value="eExam"/>

<input type="checkbox"/>	MCQ	A slide-wire potentiometer is balanced against 1.0182V standard cell at slide contact of 40.2cm. For an unknown emf the slide contact is 11.9cm. What is the emf of the unknown cell?	1.24V	0.24V	1.53V	0.30V	D	eExam
<input type="checkbox"/>	MCQ	The null condition in potentiometer experiment shows that	the potential difference under test is zero	current is varying in the circuit	current is increasing in the circuit	potential differences are balanced	D	eExam
<input type="checkbox"/>	MCQ	Which of the following is NOT correct about the experiment shown?	R1 and R2 are in series	the same current flows through R1 and R2	the potential difference across R1 and R2 is the same	the equivalent resistance of R1 and R2 is the sum of the two resistances	C	eExam
<input type="checkbox"/>	MCQ	The advantage of potentiometer over voltmeter in measurements of emf is that	the potentiometer wire is assumed to be uniform	it does not draw current from the circuit under test	the temperature of the wire must remain constant	faults may arise due to breaks or wrong connections in the circuit	B	eExam
<input type="checkbox"/>	MCQ	Which of these is not a useful precaution in an electrical experiment?	key should be removed between readings to avoid battery run-down	jockeys can be dragged or pressed sufficiently hard on resistance wires	the connections in the circuit should be tight	readings should be recorded as soon as they are obtained	B	eExam
<input type="checkbox"/>	MCQ	Which of the following is not true about a rheostat?	It is a constant current instrument	It is a variable resistor with moving contact	It is used for varying the current in a circuit	It is used for varying the resistance in a circuit	A	eExam
<input type="checkbox"/>	MCQ	In an experiment, potential difference is plotted on the ordinate (vertical axis) and current on the abscissa (horizontal axis). The slope of the graph represents	potential difference	current remains constant	resistance	resistivity	C	eExam
<input type="checkbox"/>	MCQ	In an experiment to determine the refractive index of glass using the triangular glass prism, the difference between the angle of deviation and the angle of emergence $(d - e)^{\circ}$ was plotted on the vertical axis against the angle of incidence i° on the horizontal axis. From which of the following can the value of the angle of the prism, A be found from the graph?	slope of graph	inverse of the slope of graph	intercepts on either axes	inverse of the intercept on either of the axes	C	eExam

<input type="checkbox"/>								
<input type="checkbox"/>	MCQ	In an experiment to determine the refractive index of glass using the triangular glass prism, the difference between the angle of deviation and the angle of emergence $(d - e)^{\circ}$ was plotted on the vertical axis against the angle of incidence i° on the horizontal axis. Which of the following correctly gives the sketch of the graph?	I	II	III	IV	D	eExam
<input type="checkbox"/>	MCQ	In an experiment to determine the focal length of a convex lens using an optical bench, a graph of was plotted with the values of $1/v$ on the vertical axis and $1/u$ on the horizontal axis. Which of the following correctly gives the power of the lens?	slope of the graph	inverse of the slope of the graph	intercept on either of the axes	inverse of the intercept on either of the axes	C	eExam
<input type="checkbox"/>	MCQ	Describe the image of candle positioned 20 cm in front of a concave mirror of focal length 30 cm	virtual, inverted, 12cm behind mirror and magnified 3 times	real, inverted, 12cm in front of mirror and diminished 3 times	virtual, erect, 60cm behind mirror and magnified 3 times	real, erect, 60cm in front of mirror and diminished 3 times	C	eExam
<input type="checkbox"/>	MCQ	In an experiment to determine the focal length of a convex lens using an optical bench, the object pin was placed in front of the lens between F' and $2F'$. Describe the image of the the pin as seen on the other side of the lens.	real and inverted	real and upright	virtual and erect	virtual and upright	A	eExam
<input type="checkbox"/>	MCQ	In an experiment to demonstrate how the object and images distances vary for a convex mirror, a graph with $1/u$ on the ordinate and $1/v$ on the abscissa was plotted. Which of the following figures correctly gives the shape of the graph?	I	II	III	IV	B	eExam
<input type="checkbox"/>	MCQ	In an experiment involving a spherical mirror, $1/v$ was plotted on the vertical axis and $1/u$ on the horizontal axis. What is the linear magnification?	slope of the graph	inverse of the slope of the graph	intercept on the vertical axis	intercept on the horizontal axis	B	eExam
<input type="checkbox"/>	MCQ	Which of the following is NOT true of experiments involving curved mirrors?	image distance is negative for real image	object distance is positive	image distance is negative for virtual image	focal length is negative for convex mirrors	A	eExam
<input type="checkbox"/>	MCQ	In an experiment, derived values such as those obtained from four figure tables should be recorded to at least ----- decimal places	2	3	5	7	B	eExam

<input type="checkbox"/>	MCQ	Which of the following is NOT applicable when plotting the graph of experimental data?	Lines of best fit should always be used to connect the plotted points	circled dots or crosses may be used to show plotted points	thin, sharp and continuous lines are acceptable	the scale must be chosen to make the graph occupy as small as possible of the graph page	D	eExam
<input type="checkbox"/>	MCQ	An estimate of the refractive index of glass is 1.5. If the angle of incidence is 30° the angle of refraction is	19°	60°	35°	70°	A	eExam
<input type="checkbox"/>	MCQ	The critical angle for total internal reflection at an air-water interface is approximately 48° . In which of the following situations will total internal reflection occur.	light incident in water at 44°	light incident in water at 55°	light incident in air at 40°	light incident in air at 55°	B	eExam
<input type="checkbox"/>	MCQ	In experimental observations involving rectangular glass blocks,	the angle of incidence is less than the angle of refraction in general	the angle of incidence is equal to the angle of refraction	the angle of incidence is greater than the angle of refraction when light is moving out of the block	the angle of refraction is less than the angle of incidence when light is entering the block	D	eExam
<input type="checkbox"/>	MCQ	Which of the following is NOT a precaution in optical experiments that involve glass blocks?	sharp, thin lines should be drawn to represent the rays	The glass block must be properly replaced on the traced outline	Optical pins must cluster together	Optical pins must be kept erect	C	eExam
<input type="checkbox"/>	MCQ	In an optical experiment to determine the refractive index of a glass block, a student plotted the values of the sines of the angles of incidence, $\sin i$ on the vertical axis and the values of the sines of the angles of refraction, $\sin r$ on the horizontal axis of his graph. Which of the following correctly gives the refractive index of the glass block from Snell's law using his graph?	intercept on the horizontal axis	intercept on the vertical axis	inverse of the slope of the graph	slope of the graph	D	eExam

Showing 1 to 150 of 200 entries

Previous 1 2 Next