

eExam Question Bank

Coursecode:




 Show  entries

 Search: 

<input type="checkbox"/>	Question Type ↓	Question ↑	A ↑	B ↑	C ↑	D ↑	Answer ↑	Remark ↑
<input type="checkbox"/>	FBQ	Attenuation is measured in units of <input type="text"/>	decibels	decibel				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	Attenuators used with coaxial lines are the <input type="text"/> form while attenuators for use with twisted pair are required to be the <input type="text"/> form.	unbalanced, balanced	unbalanced, balanced				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	Frequency bandwidth is expressed in units of <input type="text"/>	hertz	hertz				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	A filter in which the signal passes through an inductor, or in which a capacitor provides a path to ground, presents less attenuation to low-frequency signals than high-frequency signals and is a <input type="text"/> filter	low-pass	low-pass				<input type="button" value="eExam"/>
<input type="checkbox"/>	FBQ	Linear filters whose implementation is based on the combination of resistors (R), inductors (L) and capacitors (C) are collectively known as <input type="text"/> filters	passive	passive				<input type="button" value="eExam"/>

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	<p>For a series RLC circuit, if</p> $f = \frac{1}{2\pi\sqrt{LC}}$ <p>,</p> <p style="text-align: center;"><math>f</math></p> <p>is the</p> <input type="text"/> <p>frequency</p>	resonant	resonance				eExam
<input type="checkbox"/>	FBQ	<p>In a series RLC circuit, the capacitive reactance causes total current to</p> <input type="text"/> <p>the applies voltage.</p>	lead	lead				eExam
<input type="checkbox"/>	FBQ	<p>The electrical properties of semiconductors can be modified by addition of impurities to the pure semiconductor substrate. This process is known as</p> <input type="text"/>	doping	doping				eExam
<input type="checkbox"/>	FBQ	<p>For reactive loads, maximum power transfer takes place when the source impedance is the complex</p> <input type="text"/> <p>of the load impedance</p>	conjugate	conjugate				eExam
<input type="checkbox"/>	FBQ	<p>Electrical impedance has both magnitude and</p> <input type="text"/> <p>angle</p>	phase	phase				eExam
<input type="checkbox"/>	FBQ	<p>The impedance of a lossless idealized network element is referred to as</p> <input type="text"/>	reactance	reactance				eExam
<input type="checkbox"/>	FBQ	<p>The conduction mechanism in semiconductors is contributed to by both electrons and</p> <input type="text"/>	holes	holes				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	<p>Circuit elements which have a linear voltage to current relationship and which obey Ohm's Law are referred to as</p> <input type="text"/> <p>devices</p>	ohmic	ohmic				eExam
<input type="checkbox"/>	FBQ	<p>An electronic device that reduces the amplitude or power of a signal without appreciably distorting its waveform is called</p> <input type="text"/>	attenuator	an attenuator				eExam
<input type="checkbox"/>	FBQ	<p>An</p> <input type="text"/> <p>filter consists of two reactive elements, one in series and one in parallel</p>	L	L				eExam
<input type="checkbox"/>	FBQ	<p>A narrow region around the PN junction formed by the diffusion of majority carriers across the junction is called the</p> <input type="text"/> <p>layer.</p>	depletion	space-charge				eExam
<input type="checkbox"/>	FBQ	<p>In a linear network, having several sources (which include the equivalent source due to initial conditions), the overall response, at any point in the network, is equal to the sum of individual responses of each source considered separately, the other sources being made inoperative. This the</p> <input type="text"/> <p>theorem of electrical network</p>	superposition	superposition				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	"Insofar as load is concerned, any one-port network of resistance elements and energy sources can be replaced by a series combination of an ideal voltage source $V$ and resistance $R$ , where $V$ is the open-circuit voltage of the one-port and $R$ is the ratio of the open-circuit voltage to the short-circuit current". This is <input type="text"/> theorem	Thevenin's	Thevenin				eExam
<input type="checkbox"/>	FBQ	If a parallel combination of $12\Omega$ and $6\Omega$ resistances is connected to a series combination a $42V$ d.c. source and a $3\Omega$ resistance, the current in the $12\Omega$ resistance (to the nearest whole number) is <input type="text"/> A	2	2				eExam
<input type="checkbox"/>	FBQ	Two one-ports are <input type="text"/> if they present the same v-i characteristics	equivalent	equivalent				eExam
<input type="checkbox"/>	FBQ	The statement "the algebraic sum of the currents into a node at an instant is zero" is <input type="text"/> current	Kirchhoff's	Kirchhoff's				eExam
<input type="checkbox"/>	FBQ	Is a Klystron a Vacuum Tube? <input type="text"/>	yes	YES				eExam
<input type="checkbox"/>	FBQ	the two types of bipolar junction transistors are <input type="text"/> and <input type="text"/> transistors	NPN, PNP	PNP, NPN				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	The dual of an N Channel field effect transistor is a <input type="text"/> channel field effect transistor	P	P				eExam
<input type="checkbox"/>	FBQ	Germanium, Silicon, Gallium Arsenide and Silicon Carbide are all examples of <input type="text"/> materials	semiconductor	semiconductor				eExam
<input type="checkbox"/>	FBQ	If a twisted pair transmission line is balanced write BALANCED, otherwise write UNBALANCED in this space provided <input type="text"/>	BALANCED	BALANCED				eExam
<input type="checkbox"/>	FBQ	The theorem which is frequently called "the parallel generator theorem" is the <input type="text"/> theorem	Millman's	Millman				eExam
<input type="checkbox"/>	FBQ	Another name for Maximum Power theorem is <input type="text"/> law	Jacobi's	Jacobi				eExam
<input type="checkbox"/>	FBQ	At resonance, the <input type="text"/> and <input type="text"/> reactances of an LC circuit are equal	capacitive, inductive	inductive, capacitive				eExam
<input type="checkbox"/>	FBQ	The theorem which states that the reactance of a passive, lossless one-port network always monotonically increases with frequency is called the <input type="text"/> reactance theorem	Foster's	Foster				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	A bipolar junction transistor is basically a <input type="text"/> - terminal device	three	3				eExam
<input type="checkbox"/>	FBQ	Transistors are generally classified as <input type="text"/> and <input type="text"/> transistors	bipolar junction , field effect	field effect, bipolar junction				eExam
<input type="checkbox"/>	FBQ	The <input type="text"/> diode is used for the construction of a voltage regulator	Zener	zener				eExam
<input type="checkbox"/>	FBQ	The conection of the positive terminal of a battery to the P-side and negative terminal to the N-side of a PN junction is referred to as <input type="text"/> bias	reverse	reverse				eExam
<input type="checkbox"/>	FBQ	The process whereby a AC voltage is converted to a unidirectional (DC) voltage is refered to as <input type="text"/>	rectification	rectification				eExam
<input type="checkbox"/>	FBQ	The early electronic devices (diodes, triodes, etc) depended on <input type="text"/> effect for the generation of current carriers (electrons)	thermionic	thermionic				eExam
<input type="checkbox"/>	FBQ	The first diodes were made of <input type="text"/> tubes	vacuum	vacuum				eExam
<input type="checkbox"/>	FBQ	Energy stored in the form of a magnetic field or a moving charge in the <input type="text"/>	inductor	inductor				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	<p>Which of the following circuit quantities is employed in the storage of energy?</p> <input type="text"/> <p>(resistance, capacitance, conductance, resistivity)</p>	capacitance	capacitance				eExam
<input type="checkbox"/>	FBQ	<p>Given that <math>i = Gv</math>, where <math>i</math> is the current and <math>v</math> is the potential difference, then the unit of <math>G</math> is</p> <input type="text"/> <p>(ohms, siemens, ampres, volts)</p>	siemens	siemens				eExam
<input type="checkbox"/>	FBQ	<p>The electron gun of a cathode ray tube provides a beam of high velocity electron. If the electrons are accelerated through a potential difference of 20 000 eV over a distance of 4 cm, then the field strength is</p> <input type="text"/> <p><math>\times 10^5</math> V/m (2, 3, 4, 5)</p>	5	5				eExam
<input type="checkbox"/>	FBQ	<p>The quantity <math>\int \vec{B} \cdot d\vec{A}</math> defines the</p> <input type="text"/> <p>(magnetic flux density, electric current density, magnetic field strength, magnetic flux)</p>	magnetic flux	magnetic flux				eExam
<input type="checkbox"/>	FBQ	<p>the potential gradient is a measure of the</p> <input type="text"/> <p>(electric current, magnetic flux density, electric flux, electric field strength)</p>	electric field strength	electric field strength				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	The energy transfer capability of the flow of electric charge is determined by the <input type="text"/> through which the charge moves (resistance, potential difference, impedance, current)	potential difference	potential difference				eExam
<input type="checkbox"/>	FBQ	A circuit device which changes or information to another is called <input type="text"/> (transducer, modulator, oscillator, amplifier)	transducer	transducer				eExam
<input type="checkbox"/>	FBQ	When the dimensions of a network component s unimportant and its total effect can be considered to be concentrated at a poin, then the component can be represented by a <input type="text"/> parameter (lumped, distributed, continuous, discrete)	lumped	lumped				eExam
<input type="checkbox"/>	FBQ	A transistor <input type="text"/> <input type="text"/> device (active, linear; passive, nonlinear; passive, linear; active, non-linear)	active, non-linear	active, non-linear				eExam
<input type="checkbox"/>	FBQ	A two- terminal device is a <input type="text"/> - port (one, two, three, four)	one	one				eExam
<input type="checkbox"/>	FBQ	Transistors are <input type="text"/> -ports. (tow, three, four, one)	two	two				eExam
<input type="checkbox"/>	FBQ	A diode is a <input type="text"/> - terminal device (one, two, three, four)	two	two				eExam

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	Attenuation is measured in units of <input type="text"/>	decibels	decibel				
<input type="checkbox"/>	FBQ	Attenuators used with coaxial lines are the <input type="text"/> form while attenuators for use with twisted pair are required to be the <input type="text"/> form.	unbalanced, balanced	unbalanced, balanced				
<input type="checkbox"/>	FBQ	Frequency bandwidth is expressed in units of <input type="text"/>	hertz	hertz				
<input type="checkbox"/>	FBQ	A filter in which the signal passes through an inductor, or in which a capacitor provides a path to ground, presents less attenuation to low-frequency signals than high-frequency signals and is a <input type="text"/> filter	low-pass	low-pass				
<input type="checkbox"/>	FBQ	Linear filters whose implementation is based on the combination of resistors (R), inductors (L) and capacitors (C) are collectively known as <input type="text"/> filters	passive	passive				
<input type="checkbox"/>	FBQ	For a series RLC circuit, if $f = \frac{1}{2\pi\sqrt{LC}}$ , $f$ is the <input type="text"/> frequency	resonant	resonance				
<input type="checkbox"/>	FBQ	In a series RLC circuit, the capacitive reactance causes total current to <input type="text"/> the applies voltage.	lead	lead				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	The electrical properties of semiconductors can be modified by addition of impurities to the pure semiconductor substrate. This process is known as <input type="text"/>	doping	doping				
<input type="checkbox"/>	FBQ	For reactive loads, maximum power transfer takes place when the source impedance is the complex <input type="text"/> of the load impedance	conjugate	conjugate				
<input type="checkbox"/>	FBQ	Electrical impedance has both magnitude and <input type="text"/> angle	phase	phase				
<input type="checkbox"/>	FBQ	The impedance of a lossless idealized network element is referred to as <input type="text"/>	reactance	reactance				
<input type="checkbox"/>	FBQ	The conduction mechanism in semiconductors is contributed to by both electrons and <input type="text"/>	holes	holes				
<input type="checkbox"/>	FBQ	Circuit elements which have a linear voltage to current relationship and which obey Ohm's Law are referred to as <input type="text"/> devices	ohmic	ohmic				
<input type="checkbox"/>	FBQ	An electronic device that reduces the amplitude or power of a signal without appreciably distorting its waveform is called <input type="text"/>	attenuator	an attenuator				
<input type="checkbox"/>	FBQ	An <input type="text"/> filter consists of two reactive elements, one in series and one in parallel	L	L				

<input type="checkbox"/>							
<input type="checkbox"/>	FBQ	A narrow region around the PN junction formed by the diffusion of majority carriers across the junction is called the <input type="text"/> layer.	depletion	space-charge			
<input type="checkbox"/>	FBQ	In a linear network, having several sources (which include the equivalent source due to initial conditions), the overall response, at any point in the network, is equal to the sum of individual responses of each source considered separately, the other sources being made inoperative. This the <input type="text"/> theorem of electrical network	superposition	superposition			
<input type="checkbox"/>	FBQ	"Insofar as load is concerned, any one-port network of resistance elements and energy sources can be replaced by a series combination of an ideal voltage source $V$ and resistance $R$ , where $V$ is the open-circuit voltage of the one-port and $R$ is the ratio of the open-circuit voltage to the short-circuit current". This is <input type="text"/> theorem	Thevenin's	Thevenin			
<input type="checkbox"/>	FBQ	If a parallel combination of $12\ \Omega$ and $6\ \Omega$ resistances is connected to a series combination a $42\text{V}$ d.c. source and a $3\ \Omega$ resistance, the current in the $12\ \Omega$ resistance (to the nearest whole number) is <input type="text"/> A	2	2			

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	Two one-ports are <input type="text"/> if they present the same v-l characteristics	equivalent	equivalent				
<input type="checkbox"/>	FBQ	The statement "the algebraic sum of the currents into a node at an instant is zero" is <input type="text"/> current	Kirchhoff's	Kirchhoff's				
<input type="checkbox"/>	FBQ	Is a Klystron a Vacuum Tube? <input type="text"/>	yes	YES				
<input type="checkbox"/>	FBQ	the two types of bipolar junction transistors are <input type="text"/> and <input type="text"/> transistors	NPN, PNP	PNP, NPN				
<input type="checkbox"/>	FBQ	The dual of an N Channel field effect transistor is a <input type="text"/> channel field effect transistor	P	P				
<input type="checkbox"/>	FBQ	Germanium, Silicon, Gallium Arsenide and Silicon Carbide are all examples of <input type="text"/> materials	semiconductor	semiconductor				
<input type="checkbox"/>	FBQ	If a twisted pair transmission line is balanced write BALANCED, otherwise write UNBALANCED in this space provided <input type="text"/>	BALANCED	BALANCED				
<input type="checkbox"/>	FBQ	The theorem which is frequently called "the parallel generator theorem" is the <input type="text"/> theorem	Millman's	Millman				

<input type="checkbox"/>							
<input type="checkbox"/>	FBQ	Another name for Maximum Power theorem is <input type="text"/> law	Jacobi's	Jacobi			
<input type="checkbox"/>	FBQ	At resonance, the <input type="text"/> and <input type="text"/> reactances of an LC circuit are equal	capacitive, inductive	inductive, capacitive			
<input type="checkbox"/>	FBQ	The theorem which states that the reactance of a passive, lossless one-port network always monotonically increases with frequency is called the <input type="text"/> reactance theorem	Foster's	Foster			
<input type="checkbox"/>	FBQ	A bipolar junction transistor is basically a <input type="text"/> - terminal device	three	3			
<input type="checkbox"/>	FBQ	Transistors are generally classified as <input type="text"/> and <input type="text"/> transistors	bipolar junction , field effect	field effect, bipolar junction			
<input type="checkbox"/>	FBQ	The <input type="text"/> diode is used for the construction of a voltage regulator	Zener	zener			
<input type="checkbox"/>	FBQ	The conection of the positive terminal of a battery to the P-side and negative terminal to the N-side of a PN junction is referred to as <input type="text"/> bias	reverse	reverse			

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	The process whereby a AC voltage is converted to a unidirectional (DC) voltage is referred to as <input type="text"/>	rectification	rectification				
<input type="checkbox"/>	FBQ	The early electronic devices (diodes, triodes, etc) depended on <input type="text"/> effect for the generation of current carriers (electrons)	thermionic	thermionic				
<input type="checkbox"/>	FBQ	The first diodes were made of <input type="text"/> tubes	vacuum	vacuum				
<input type="checkbox"/>	FBQ	Energy stored in the form of a magnetic field or a moving charge in the <input type="text"/>	inductor	inductor				
<input type="checkbox"/>	FBQ	Which of the following circuit quantities is employed in the storage of energy? <input type="text"/> (resistance, capacitance, conductance, resistivity)	capacitance	capacitance				
<input type="checkbox"/>	FBQ	Given that $i = Gv$ , where $i$ is the current and $v$ is the potential difference, then the unit of $G$ is <input type="text"/> (ohms, siemens, ampres, volts)	siemens	siemens				
<input type="checkbox"/>	FBQ	The electron gun of a cathode ray tube provides a beam of high velocity electron. If the electrons are accelerated through a potential difference of 20 000 eV over adistance of 4 cm, then the field strength is <input type="text"/> $\times 10^5$ V/m (2, 3, 4, 5)	5	5				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	<p>The quantity <math>\int \vec{B} \cdot d\vec{A}</math> defines the</p> <input type="text"/> <p>(magnetic flux density, electric current density, magnetic field strength, magnetic flux)</p>	magnetic flux	magnetic flux				
<input type="checkbox"/>	FBQ	<p>the potential gradient is a measure of the</p> <input type="text"/> <p>(electric current, magnetic flux density, electric flux, electric field strength)</p>	electric field strength	electric field strength				
<input type="checkbox"/>	FBQ	<p>The energy transfer capability of the flow of electric charge is determined by the</p> <input type="text"/> <p>through which the charge moves (resistance, potential difference, impedance, current)</p>	potential difference	potential difference				
<input type="checkbox"/>	FBQ	<p>A circuit device which changes or information to another is called</p> <input type="text"/> <p>(transducer, modulator, oscillator, amplifier)</p>	transducer	transducer				
<input type="checkbox"/>	FBQ	<p>When the dimensions of a network component s unimportant and its total effect can be considered to be concentrated at a poin, then the component can be represented by a</p> <input type="text"/> <p>parameter (lumped, distributed, continuous, discrete)</p>	lumped	lumped				
<input type="checkbox"/>	FBQ	<p>A transistor</p> <input type="text"/> <p>,</p> <input type="text"/> <p>device (active, linear; passive, nonlinear; passive, linear; active, non-linear)</p>	active, non-linear	active, non-linear				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	A two- terminal device is a <input type="text"/> - port (one, two, three, four)	one	one				
<input type="checkbox"/>	FBQ	Transistors are <input type="text"/> -ports. (tow, three, four, one)	two	two				
<input type="checkbox"/>	FBQ	A diode is a <input type="text"/> - terminal device (one, two, three, four)	two	two				
<input type="checkbox"/>	FBQ	Attenuation is measured in units of <input type="text"/>	decibels	decibel				
<input type="checkbox"/>	FBQ	Attenuators used with coaxial lines are the <input type="text"/> form while attenuators for use with twisted pair are required to be the <input type="text"/> form.	unbalanced, balanced	unbalanced, balanced				
<input type="checkbox"/>	FBQ	Frequency bandwidth is expressed in units of <input type="text"/>	hertz	hertz				
<input type="checkbox"/>	FBQ	A filter in which the signal passes through an inductor, or in which a capacitor provides a path to ground, presents less attenuation to low-frequency signals than high-frequency signals and is a <input type="text"/> filter	low-pass	low-pass				
<input type="checkbox"/>	FBQ	Linear filters whose implementation is based on the combination of resistors (R), inductors (L) and capacitors (C) are collectively known as <input type="text"/> filters	passive	passive				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	For a series RLC circuit, if $f = \frac{1}{2\pi\sqrt{LC}}$ , $f$ is the <input type="text"/> frequency	resonant	resonance				
<input type="checkbox"/>	FBQ	In a series RLC circuit, the capacitive reactance causes total current to <input type="text"/> the applies voltage.	lead	lead				
<input type="checkbox"/>	FBQ	The electrical properties of semiconductors can be modified by addition of impurities to the pure semiconductor substrate. This process is known as <input type="text"/>	doping	doping				
<input type="checkbox"/>	FBQ	For reactive loads, maximum power transfer takes place when the source impedance is the complex <input type="text"/> of the load impedance	conjugate	conjugate				
<input type="checkbox"/>	FBQ	Electrical impedance has both magnitude and <input type="text"/> angle	phase	phase				
<input type="checkbox"/>	FBQ	The impedance of a lossless idealized network element is referred to as <input type="text"/>	reactance	reactance				
<input type="checkbox"/>	FBQ	The conduction mechanism in semiconductors is contributed to by both electrons and <input type="text"/>	holes	holes				
<input type="checkbox"/>	FBQ	Circuit elements which have a linear voltage to current relationship and which obey Ohm's Law are referred to as <input type="text"/> devices	ohmic	ohmic				

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	An electronic device that reduces the amplitude or power of a signal without appreciably distorting its waveform is called <input type="text"/>	attenuator	an attenuator				
<input type="checkbox"/>	FBQ	An <input type="text"/> filter consists of two reactive elements, one in series and one in parallel	L	L				
<input type="checkbox"/>	FBQ	A narrow region around the PN junction formed by the diffusion of majority carriers across the junction is called the <input type="text"/> layer.	depletion	space-charge				
<input type="checkbox"/>	FBQ	In a linear network, having several sources (which include the equivalent source due to initial conditions), the overall response, at any point in the network, is equal to the sum of individual responses of each source considered separately, the other sources being made inoperative. This the <input type="text"/> theorem of electrical network	superposition	superposition				
<input type="checkbox"/>	FBQ	"Insofar as load is concerned, any one-port network of resistance elements and energy sources can be replaced by a series combination of an ideal voltage source $V$ and resistance $R$ , where $V$ is the open-circuit voltage of the one-port and $R$ is the ratio of the open-circuit voltage to the short-circuit current". This is <input type="text"/> theorem	Thevenin's	Thevenin				

<input type="checkbox"/>							
<input type="checkbox"/>	FBQ	<p>If a parallel combination of <math>12\Omega</math> and <math>6\Omega</math> resistances is connected to a series combination a <math>42V</math> d.c. source and a <math>3\Omega</math> resistance, the current in the <math>12\Omega</math> resistance (to the nearest whole number) is</p> <input type="text"/> <p>A</p>	2	2			
<input type="checkbox"/>	FBQ	<p>Two one-ports are</p> <input type="text"/> <p>if they present the same v-i characteristics</p>	equivalent	equivalent			
<input type="checkbox"/>	FBQ	<p>The statement "the algebraic sum of the currents into a node at an instant is zero" is</p> <input type="text"/> <p>current</p>	Kirchhoff's	Kirchhoff's			
<input type="checkbox"/>	FBQ	<p>Is a Klystron a Vacuum Tube?</p> <input type="text"/>	yes	YES			
<input type="checkbox"/>	FBQ	<p>the two types of bipolar junction transistors are</p> <input type="text"/> <p>and</p> <input type="text"/> <p>transistors</p>	NPN, PNP	PNP, NPN			
<input type="checkbox"/>	FBQ	<p>The dual of an N Channel field effect transistor is a</p> <input type="text"/> <p>channel field effect transistor</p>	P	P			
<input type="checkbox"/>	FBQ	<p>Germanium, Silicon, Gallium Arsenide and Silicon Carbide are all examples of</p> <input type="text"/> <p>materials</p>	semiconductor	semiconductor			

<input type="checkbox"/>							
<input type="checkbox"/>	FBQ	If a twisted pair transmission line is balanced write BALANCED, otherwise write UNBALANCED in this space provided <input type="text"/>	BALANCED	BALANCED			
<input type="checkbox"/>	FBQ	The theorem which is frequently called "the parallel generator theorem" is the <input type="text"/> theorem	Millman's	Millman			
<input type="checkbox"/>	FBQ	Another name for Maximum Power theorem is <input type="text"/> law	Jacobi's	Jacobi			
<input type="checkbox"/>	FBQ	At resonance, the <input type="text"/> and <input type="text"/> reactances of an LC circuit are equal	capacitive, inductive	inductive, capacitive			
<input type="checkbox"/>	FBQ	The theorem which states that the reactance of a passive, lossless one-port network always monotonically increases with frequency is called the <input type="text"/> reactance theorem	Foster's	Foster			
<input type="checkbox"/>	FBQ	A bipolar junction transistor is basically a <input type="text"/> - terminal device	three	3			
<input type="checkbox"/>	FBQ	Transistors are generally classified as <input type="text"/> and <input type="text"/> transistors	bipolar junction , field effect	field effect, bipolar junction			

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	The <input type="text"/> diode is used for the construction of a voltage regulator	Zener	zener				
<input type="checkbox"/>	FBQ	The connection of the positive terminal of a battery to the P-side and negative terminal to the N-side of a PN junction is referred to as <input type="text"/> bias	reverse	reverse				
<input type="checkbox"/>	FBQ	The process whereby a AC voltage is converted to a unidirectional (DC) voltage is referred to as <input type="text"/>	rectification	rectification				
<input type="checkbox"/>	FBQ	The early electronic devices (diodes, triodes, etc) depended on <input type="text"/> effect for the generation of current carriers (electrons)	thermionic	thermionic				
<input type="checkbox"/>	FBQ	The first diodes were made of <input type="text"/> tubes	vacuum	vacuum				
<input type="checkbox"/>	FBQ	Energy stored in the form of a magnetic field or a moving charge in the <input type="text"/>	inductor	inductor				
<input type="checkbox"/>	FBQ	Which of the following circuit quantities is employed in the storage of energy? <input type="text"/> (resistance, capacitance, conductance, resistivity)	capacitance	capacitance				

<input type="checkbox"/>							
<input type="checkbox"/>	FBQ	<p>Given that <math>I = Gv</math>, where <math>I</math> is the current and <math>v</math> is the potential difference, then the unit of <math>G</math> is</p> <input type="text"/> <p>(ohms, siemens, ampres, volts)</p>	siemens	siemens			
<input type="checkbox"/>	FBQ	<p>The electron gun of a cathode ray tube provides a beam of high velocity electron. If the electrons are accelerated through a potential difference of 20 000 eV over a distance of 4 cm, then the field strength is</p> <input type="text"/> <p><math>\times 10^5</math> V/m (2, 3, 4, 5)</p>	5	5			
<input type="checkbox"/>	FBQ	<p>The quantity <math>\int \vec{B} \cdot d\vec{A}</math> defines the</p> <input type="text"/> <p>(magnetic flux density, electric current density, magnetic field strength, magnetic flux)</p>	magnetic flux	magnetic flux			
<input type="checkbox"/>	FBQ	<p>the potential gradient is a measure of the</p> <input type="text"/> <p>(electric current, magnetic flux density, electric flux, electric field strength)</p>	electric field strength	electric field strength			
<input type="checkbox"/>	FBQ	<p>The energy transfer capability of the flow of electric charge is determined by the</p> <input type="text"/> <p>through which the charge moves (resistance, potential difference, impedance, current)</p>	potential difference	potential difference			

<input type="checkbox"/>								
<input type="checkbox"/>	FBQ	A circuit device which changes or information to another is called <input type="text"/> (transducer, modulator, oscillator, amplifier)	transducer	transducer				
<input type="checkbox"/>	FBQ	When the dimensions of a network component s unimportant and its total effect can be considered to be concentrated at a poin, then the component can be represented by a <input type="text"/> parameter (lumped, distributed, continuous, discrete)	lumped	lumped				
<input type="checkbox"/>	FBQ	A transistor <input type="text"/> , <input type="text"/> device (active, linear; passive, nonlinear; passive, linear; active, non-linear)	active, non-linear	active, non-linear				
<input type="checkbox"/>	FBQ	A two- terminal device is a <input type="text"/> - port (one, two, three, four)	one	one				
<input type="checkbox"/>	FBQ	Transistors are <input type="text"/> -ports. (tow, three, four, one)	two	two				
<input type="checkbox"/>	FBQ	A diode is a <input type="text"/> - terminal device (one, two, three, four)	two	two				

Showing 1 to 150 of 300 entries

Previous **1** 2 Next