



NATIONAL OPEN UNIVERSITY OF NIGERIA
PLOT 91, CADASTRAL ZONE, NNAMDI AZIKIWE EXPRESSWAY, JABI - ABUJA
FACULTY OF SCIENCES

DEPARTMENT OF PURE AND APPLIED SCIENCE


OCT/NOV 2019 EXAMINATIONS

COURSE CODE: PHY 308
COURSE TITLE: ELECTRONICS I
CREDIT UNIT: 2
TIME ALLOWED: (2 HRS)

INSTRUCTION: Answer question 1 and any other three questions

QUESTION 1

- a) i- State the function and basic properties of amplifier. **2 marks**
ii- State the typical maximum efficiencies for class A, class B and class AB amplifiers. **3 marks**
- b) i- With the aid of diagram, describe a half wave rectifier circuit. **3 marks**
ii- Briefly explain the operating conditions of the transistor when used as a switch for both "Fully-OFF" and "Fully-ON" **2 marks**
- c) i- Differentiate between *gain margin* and *phase margin* **2 marks**
ii- What is meant by power supply? (**2marks**). Enumerate the sources of electricity. **3 marks**
- d) i- Explain the terms Digital and analogue IC's **3 marks**
ii- For dc fixed-bias configuration in the figure below, Determine the values of I_{BQ} , I_{CQ} , V_{CEQ} , V_B , V_C and V_{BC} . What is your comment on value of V_{BC} obtained? **5 marks**

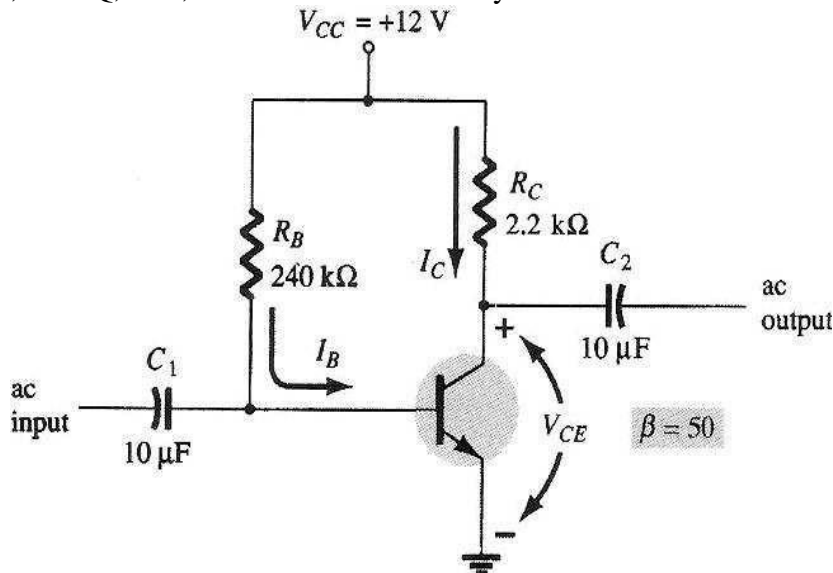

QUESTION 2

- (a) Sketch a diagram of an Ideal Amplifier Model. **4 marks**
- (b) Determine the Voltage, Current and Power Gain of an amplifier that has an input signal of $1mA$ at $10mV$ and a corresponding output signal of $10mA$ at $1V$. Also, express all three gains in decibels. **3 marks**
- (c) Briefly describe the operation of a Class A amplifier **4 marks**
- (d) Draw a complete Transistor Characteristics showing Load Line and Q- Point **4 marks**

QUESTION 3

- (a) Briefly explain the term "frequency stability of an oscillator" and name any six factors responsible for it. **5 marks**
- (b) Explain any four (4) factors that affect frequency stability of an oscillator. **4 marks**
- (c) State and briefly explain the factors upon which the frequency of time-period of the oscillatory current depends. **2 marks**
- (d) Give any four (4) examples of Non sinusoidal wave forms and state the use of each **4 marks**

QUESTION 4

- (a) Explain the function of a rectifier circuit in a dc supply unit. **3marks**
- (b) What do you understand by Amplifier efficiency? **3 marks**
- (c) What are the five (5) types of Amplifier Class? Explain any **one** of them. **6 marks**
- (d) What is an operational amplifier (op-amp)? **3 marks**

QUESTION 5

- (a) State any four (3) applications of resonance effect. **3 marks**
- (b) With the aid of a block diagram, list and explain the components of a dc supply unit. **4 marks**
- (c) Draw the circuit diagram of the Half-wave, Full-wave and Full-wave Bridge rectifier circuits and indicate the respective input and output waveforms. **3 marks**
- (d) What is a Filter circuit? Draw a block diagram of a filter circuit. **5 marks**