



**NATIONAL OPEN UNIVERSITY OF NIGERIA**  
**PLOT 91, CADASTRAL ZONE, NNAMDI AZIKWE EXPRESSWAY, JABI, ABUJA**  
**FACULTY OF SCIENCES**  
**DEPARTMENT OF COMPUTER SCIENCE**  
**OCTOBER, 2019 EXAMINATIONS**

**COURSE CODE: CIT344**

**COURSE TITLE: INTRODUCTION TO COMPUTER DESIGN**

**CREDIT: 3 UNITS**

**TIME ALLOWED: 2½ HOURS**

**INSTRUCTION: ANSWER QUESTION 1 AND ANY OTHER FOUR (4) QUESTIONS**

1a) Write short notes on the following:

i) BCD (4 marks)

ii) Gray codes (3 marks)

b) State four reasons for memory expansion (4 marks)

c) State the various characteristics Finite State Machines (FSMs) share (4 marks)

d) List the flip-flop characteristics (2½ marks)

e) A processor has a 32 bits wide address bus.

(i) What is the total memory location that the processor can access? (2 marks)

(ii) What is the total memory size if all the memory locations are available to the processor?  
(2½ marks)

2a) Write short notes on Combinational logic circuit. (3 marks)

b) Identify the ways a Combinational logic circuit can be analysed. (3 marks)

c) How is a Combinational logic circuit designed? (4 marks)

d) What is a procedure in assembly language programming? (2 marks)

3a) Construct a full-adder function table and its corresponding implementation. (6 marks)

(b) Describe the various ways that pipelining improves performance? (6 marks)

4a) State the two basic operations performed on memories (2 marks)

b) Enumerate the signals typically used to support the basic operations performed on memories.  
(6 marks)

c) Suppose SRAM cost ₦250 per MB for an access time of 5ns, DRAM cost ₦100 per MB with an access time of 60ns, and the disk space costs ₦100 per GB with an access time of 7ms. Assuming we have a memory system with 256Kb of cache SRAM, 128MB of main memory DRAM, and 1GB of virtual memory (implemented as disk), calculate total cost of the memory system (4 marks)

5a) Differentiate between a multiplexer and a demultiplexer. **(6 marks)**

b) Provide suitable diagrams in support of your answer in **(a)** above. **(3 marks)**

c) What are register files? **(3 marks)**

6a) Discuss the typical applications of encoders and decoders. **(7 marks)**

b) Using diagram only, show how interrupts are resolved with 2-to-4 priority encoders. **(5 marks)**