



**NATIONAL OPEN UNIVERSITY OF NIGERIA**  
**PLOT 91, CADASTRAL ZONE, NNAMDI AZIKIWE EXPRESSWAY, JABI - ABUJA**  
**FACULTY OF SCIENCES**

**DEPARTMENT OF PURE AND APPLIED SCIENCE**

**2021\_1 EXAMINATIONS**

**COURSE CODE:** PHY405  
**COURSE TITLE:** ELECTRONICS III  
**CREDIT UNIT:** 3  
**TIME ALLOWED:** (2½ HRS)


**INSTRUCTION:** *Answer question 1 and any other four questions*

**QUESTION 1**

- a. Differentiate between BCD code and ASCII code **4 marks**
- b. What is the HEX equivalent of  $110010101001111_2$ ? **3 marks**
- c. What is the binary equivalent of  $6F10_{16}$  and  $BA6_{16}$ ? **4 marks**
- d. Obtain the decimal equivalent of  $1BE2_{16}$  **5 marks**
- e. What is the hex equivalent of  $327_8$ ? **2 marks**
- f. A 5-bit DAC produces a 20mV output for a digital input of 10110. What will  $V_{out}$  be for a digital input of 11011? **2 marks**
- g. Convert  $672.278$  into its binary equivalent. **2 marks**

**QUESTION 2**

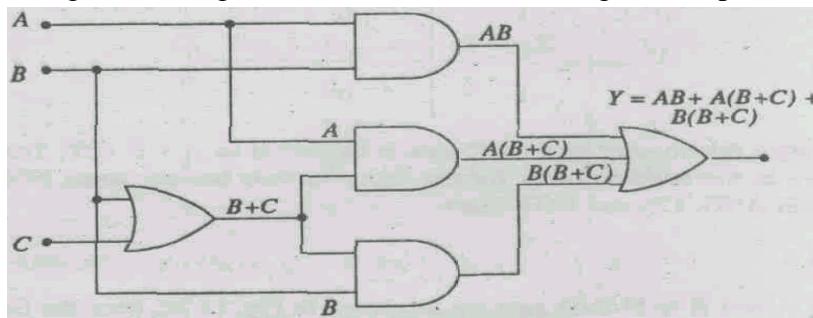- a. Using below diagram estimate the Boolean Algebra output Y



A	0	0	0	0	1	1	1	1
B	0	0	1	1	0	0	1	1
C	0	1	0	1	0	1	0	1
Y								

**9 marks**

- b. A 4-bit DAC produces an output 7v for 1110. What is the smallest change in its output voltage? Find the output voltage for 1001.

**3 marks**

**12 marks**

### QUESTION 3

- a. Define deflection sensitivity. **2 marks**
- b. Given that the deflection plates of CRT described by two geometric parameters: length (L) of the plate and the plate separated (d) and its action depends on the intensity of the electric field ( $E_d$ ),  $E_d = V_d / d$  where the field exerted on a force  $F = E_d Q$ . Show that the deflection sensitivity is given as:

$$\frac{V_d}{y} = \frac{2V_a f}{RL} \quad \mathbf{10 \text{ marks}}$$

**12 marks**

### QUESTION 4

- a. Describe the function of a generator. **4 marks**
- b. Explain the functioning of a Buffer and controlled buffer register with the aid of a well labelled diagram **8 marks**

**12 marks**

### QUESTION 5

- a. Describe in detail, the functioning of the differential-amplifier type electronic voltmeter **5 marks**
- b. Given a difference amplifier type of FET voltmeter, find the ammeter current under the following

$$V_1 = 1 \text{ V}, R_D = 10 \text{ k}\Omega, r_d = 100 \text{ k}\Omega, R_m = 50 \text{ M}\Omega, g_m = 0.005 \text{ Siemens} \quad \mathbf{7}$$

**marks**

**12 marks**

### QUESTION 6

- a. Differentiate between Asynchronous (ripple) counter and synchronous counter. Why is asynchronous counter slower compared to synchronous counter? **6 marks**
- b. If the frequency is 100kHz, what will be the output frequency of the third flip-flop of a ripple counter?

**6 marks**

**12 marks**